

Blinking LED

Project

Making an LED blink

Description

Within this tutorial you are going to make an LED blink.

Equipment You Will Need


- Raspberry pi and an SD card
- Mouse and Keyboard
- Monitor and HDMI cable
- 1 x Red LED
- 2 x male to female jumper wires
- 1 x 400 point breadboard
- Power supply
- 1 x 330Ω resistor

The Parts To Be Used

Within this section I will go through how the parts that we are going to use work and how they should be connected.

The Breadboard

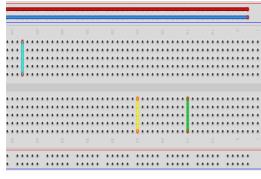The breadboard is used to connect electronics together instead of soldering. The breadboard is often used in prototyping a product.



The red line connects all the dots within this row.

The blue line connects all the dots within this row.

The turquoise line connects all the dots within this column, but is not connected to either the yellow or green lines

The yellow line connects all the dots within this column, but is not connected to either the green or the turquoise lines.



The green Line connects all the dots within this column, but is not connected to either the yellow or turquoise lines.

The LED's



LED stands for Light Emitting Diode. They glow when electricity is passed through them. When looking at LED's you will notice that there is one leg longer than the other. The longer leg known as the anode is connected to the positive supply of the circuit. The shorter leg known as the cathode is connected the the negative side of the circuit also known as ground.

If you connect the LED's the wrong way round this is not the end of the world because you will not damage them, they just will not light up.

The Resistors



Resistors limit the amount of current that can flow through an electrical circuit. Resistors are measured in ohms Ω , The larger the resistance the more the current is limited.

Resistors can be identified by the coloured bands along the body. For example the resistor that we are using is 330Ω , this is identified by orange, orange, brown then gold.

We have to use resistors to connect the LED's to the raspberry pi, or the LED's will pull too much current from the raspberry pi and this will cause the raspberry pi to stop working.

The resistors can be connected any way round because the current of the electricity will flow both ways.

The Jumper Wires



Jumper wires are used on breadboards to jump from one connection to another. The jumper wires we are using are called male to female jumper wires. The end with the pin on it will go into a hole on the breadboard, and the end with the hole will connect to a GPIO pin on our raspberry pi.


Making The Circuit

To make the circuit it is always best to have the raspberry pi turned off at this stage.

The first thing we are going to do is take a look at the GPIO (General Purpose Input Output) pins.




Model B+ & Raspberry Pi 2

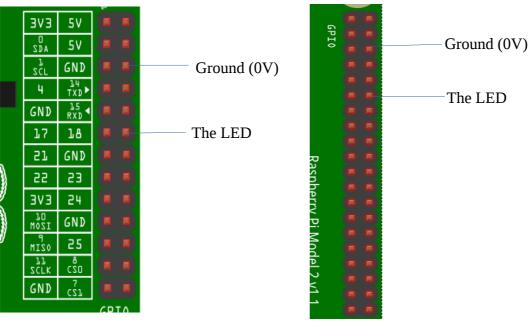

It is through the GPIO pins that the raspberry pi can control and even monitor the outside world by being connected into an electronic circuit. The raspberry pi can control LED's Motors, button presses and even buzzers.

The diagrams above show the pin layouts of the model A and B on the left and Models A+, B+ and the raspberry pi 2 on the right. I have marked out the pins we will be using and what will be connected to them.

We are now ready to set up our circuit.

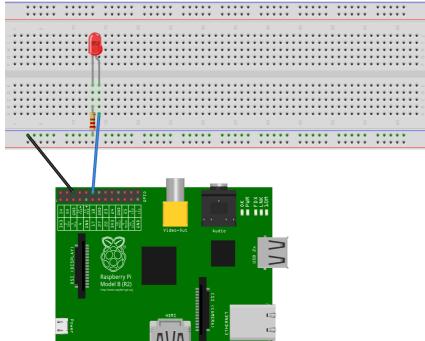

- 1. Put the LED into the breadboard with the longer leg on the right hand side.
- 2. Connect the resistor in between the short leg of the LED and the common ground rail, which is the second row from the bottom.
- 3. Take a jumper wire and connect the end with the pin into the common ground rail and the side with the hole over the ground pin on the raspberry pi.
- 4. Take the second jumper wire and connect the end with the pin into the same column as the longer leg of


fritzing



the LED and the side with the hole onto pin 18 on the raspberry pi.

Setting Up The Raspberry Pi

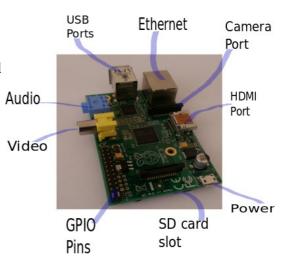- Plug in your SD card or Micro SD card depending on the raspberry pi you have
- ▶ Plug one end of the HDMI cable into the raspberry pi and the other end into the monitor
- Plug in the mouse to one of the USB ports
- ▶ Plug the keyboard into another USB port
- plug in the power supply into the micro USB port.




After you have connected all the wires and inserted your SD card, your pi should look a little like this.



After the raspberry pi has finished booting, you will either end up in the command line interface (CLI) as in the picture below on the right or in the graphical user interface (GUI) as the picture below on the left. If you see the CLI then you will need to:

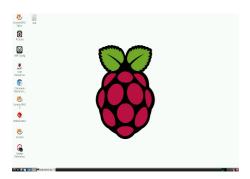- Type the user name "pi"
- Type the password. The default password is "raspberry"



```
1. If Clearing A special is executed by the control of the control
```



The first thing we need to do is open up a terminal window.

If you did my last tutorial you will remember we created a Python directory, so all we need to do now is change into that directory by typing cd Python

Next we need to create a new text file, to do that type nano Blink.py

We are now ready to type some code. The code is in red and the text in black explains what the code does.

import Rpi.GPIO as GPIO Importing the raspberry pi GPIO library as

GPIC

import time Importing the time library for timing functions

GPIO.setmode (GPIO.BCM) Setting the naming convention for the GPIO

pins

GPIO.setwarnings (False)

Telling python not to print GPIO warning

messages to the screen

GPIO.setup (18, GPIO.OUT)

Set up pin 18 as an output

GPIO.output (18, GPIO.HIGH)

Turning the LED on

time.sleep (1) Pause for 1 second

GPIO.output (18, GPIO.LOW)

Turning the LED off

time.sleep (1) Pause for 1 second

GPIO.output (18, GPIO.HIGH)

Turning the LED on

Time.sleep (1) Pause for 1 second

GPIO.Output (18, GPIO.LOW)

Tunring the LED off

GPIO.cleanup () Set the GPIO pins back to default

Once you have checked the code for any mistakes, save the code and exit the text editor by pressing ctrl+X then y then enter.

Running The Code

To run the program type sudo python Blink.py

That is all for this tutorial please join me again for the next one

Happy coding from the RaspiKidd



You can also find all my tutorials on my website: www.raspikidd.me.uk, where you can find my links to facebook and twitter.

If you have any questions please leave a comment tweet post on facebook or just email me. The email address is at the bottom of the page.